

BRAC UNIVERSITY
Department of Computer Science and Engineering
CSE 260: Digital Logic Design

Examination: **Quiz 2**
 Duration: 25 Minutes

Semester: Spring2025
 Full Marks: 15

Answer the following questions. You **MUST** show your workings/calculations where applicable.
 Figures in the right margin indicate marks.

Name:	ID:	Section:
-------	-----	----------

1. CO2	Convert the following function to its corresponding canonical POS form using boolean algebraic formulas and find the max terms: $F(D, B, A, C) = A' + B + C' + AC$ [5+3]
2. CO2	Simplify the following function to minimum literals: $F(A, B, C, D) = \sum(0, 1, 3, 4, 6, 7, 9, 10, 11, 14, 15)$ [2+5]

$$\begin{aligned}
 1. \quad F(D, C, A, B) &= A' + B + C' + AC \\
 &= (\underline{A'} + B + C' + \underline{A}) (\underline{A'} + B + \underline{C'} + \underline{C}) \\
 &= (B + C' + 1) (A' + B + 1) \\
 &= 1 \cdot 1 = 1
 \end{aligned}$$

So, there is no max term.

2.

$$\begin{aligned}
 F(A, B, C, D) &= \sum(0, 1, 3, 4, 6, 7, 9, 10, 11, 14, 15) \\
 &= \underline{A'B'C'D'} + \underline{A'B'C'D} + \underline{A'B'CD} + \underline{A'BC'D'} + \underline{A'BCD'} + \underline{A'BCD} + \underline{AB'C'D} + \underline{AB'C'D'} + \underline{AB'CD} + \underline{ABCD'} + \underline{ABCD} \\
 &= A'C'D'(B'+B) + B'D(\underline{A'C'} + \underline{A'C} + \underline{AC'} + \underline{AC}) + BC(\underline{A'D'} + \underline{A'D} + \underline{AD'} + \underline{AD}) + AB'C'D' \\
 &= A'C'D' + B'D(A'+A) + BC(A'+A) + AB'C'D' \\
 &= A'C'D' + \underline{B'D} + BC + \underline{AB'C'D'} \\
 &= A'C'D' + B'(D+ACD') + BC \\
 &= A'C'D' + B'(D+AC)(D+D') + BC \\
 &= A'C'D' + B'(D+AC) + BC \\
 &= A'C'D' + B'D + \underline{AB'C} + \underline{BC} \\
 &= A'C'D' + B'D + C(B+AB') \\
 &= A'C'D' + B'D + C(A+B)(B+B') \\
 &= A'C'D' + B'D + AC + BC \quad (A+m)
 \end{aligned}$$