

# Sequential Circuit Analysis

⇒ Circuit diagram → State diagram

Steps:

(i) Find how many Flip-Flop(s) are there.

(ii) Determine,

(i) Present States. (number of present states = number of FlipFlop in the circuit)

(ii) Next States . (number of next states = number of FlipFlop in the circuit)

(iii) Input (FlipFlop inputs and external input)

(iv) Output (External output if any)

(iii) Find the equations for


(i) All the flipflop inputs.

(ii) External output (if any)


(iv) Construct the **State table** - according to the equations you  
created in step(iii)

(v) Extend the **State** table and find next states from the flipflop  
input values. [Use **characteristic** table to do so].

(vi) Finally draw the state diagram .

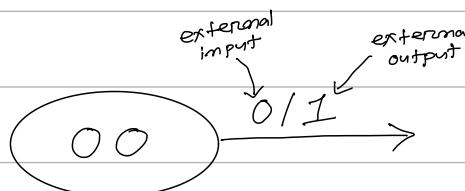

Draw the State Diagram:

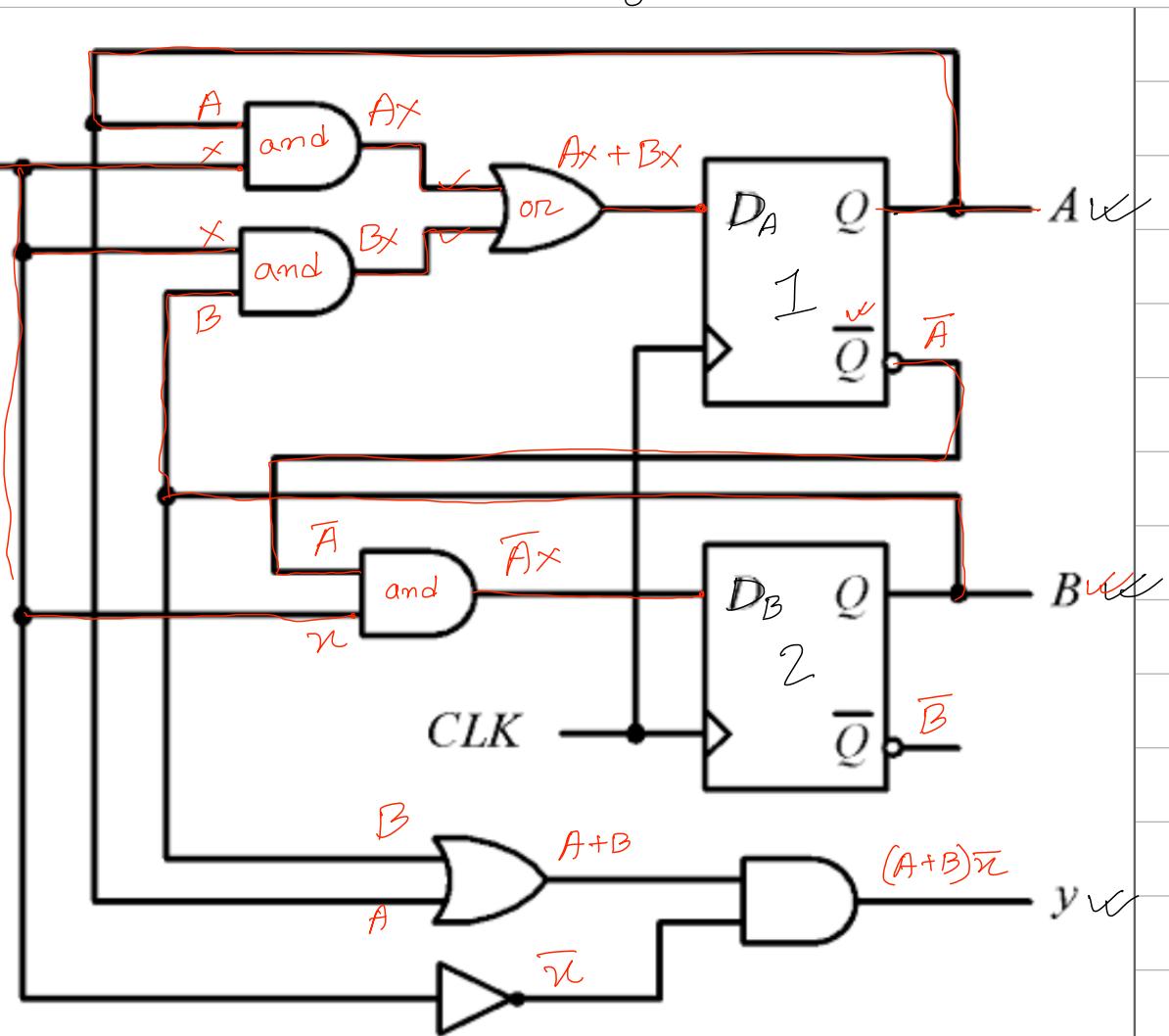

Present state:  $A, B$  ( $A(t), B(t)$ )

Next state :  $A^+, B^+$  ( $A(t+1), B(t+1)$ )

Input :  $D_A, D_B, x$

Output :  $y$

$$\text{Equations : } D_A = Ax + Bx \quad \checkmark$$


$$D_B = \bar{A}x \quad \checkmark$$

$$y = (A+B)\bar{x} \quad \checkmark$$

Present state of F.F-1      Present state of F.F-2      Ext. imp.

	A	B	$\pi$	$D_A$	$D_B$	$y$
1	0	0	0✓	0	0	0
1	0	0	1	0	1	0
1	0	1	0-	0	0	1
1	0	1	1	1	1	0
	1	0	0	0	0	1
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	1	1	0	0	0

Characteristic table

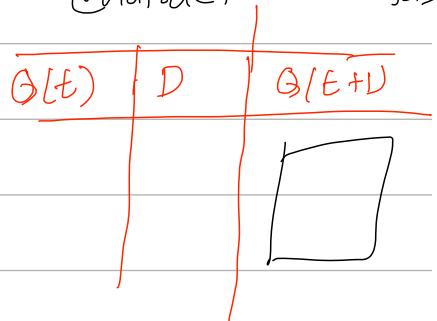

Characteristic table:

A	B	$\pi$	$D_A$	$D_B$	$y$	$A^+$	$B^+$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	0	0	1	0	0
0	1	1	1	1	0	1	1
1	0	0	0	0	1	0	0
1	0	1	1	0	0	1	0
1	1	0	0	0	1	0	0
1	1	1	1	0	0	1	0


Characteristic table:

$A / G(t)$	$D / D_B$	$G(t+1) / A^+$
0	0✓	0
0	1✓	1
1	0✓	0
1	1✓	1

$$2 \rightarrow AB \rightarrow y$$

ABC

(0 - Z)

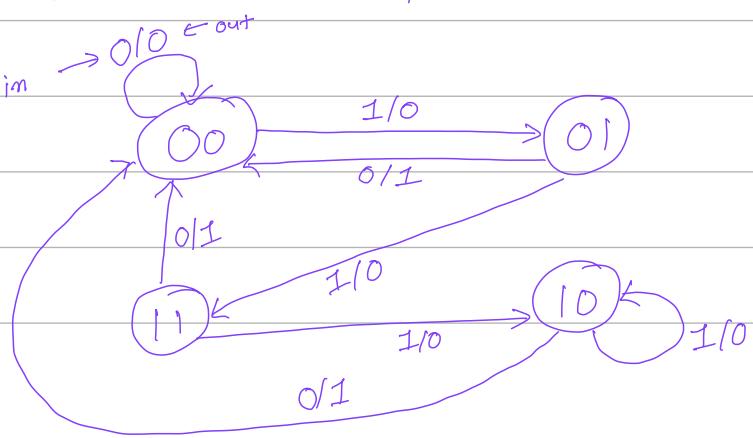



## State Diagram to Circuit:

(i) Draw the state table from the state diagram.

(ii) Extend the table and figureout the input(s) of the flip-flops.


use excitation table  
to do so.

(iii) Draw K-map(s) for all the flip-flop input(s) and external output (if any exists)

(iv) Draw the diagram.

→ No. of Flip-Flop = No. of present states.

D Flip-Flip

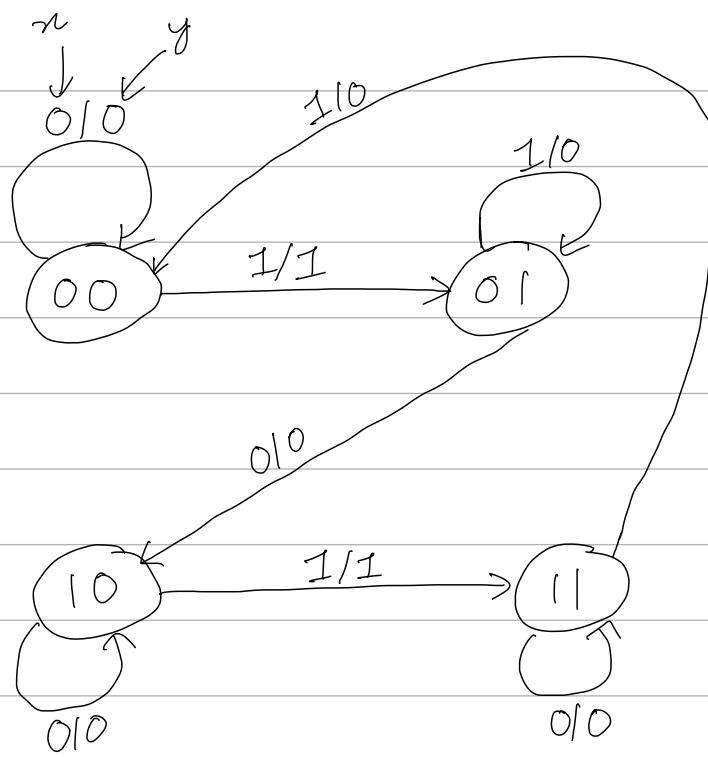

$$\begin{array}{c} A \\ \backslash \\ \begin{array}{c} 0 \\ 0 \end{array} \\ / \\ \begin{array}{c} 1 \\ 1 \end{array} \end{array} \quad \begin{array}{c} B \\ \backslash \\ \begin{array}{c} 0 \\ 0 \end{array} \\ / \\ \begin{array}{c} 1 \\ 1 \end{array} \end{array}$$

2 F.F

$\rightarrow$  K-map


<u>Pre</u>	<u>Net</u>	<u>ext<sup>+</sup> output</u>					
A <sub>-</sub>	B <sub>-</sub>	X <sub>-</sub>	A <sup>+</sup>	B <sup>+</sup>	Y	D <sub>A</sub>	D <sub>B</sub>
0	0	0	0	0	0	0	0
0	0	1	0	1	1✓	0	1
0	1	0	1	0	0	1	0
0	1	1	0	1	0	0	1
1	0	0	1	0	0	1	0
1	0	1	1	1	1✓	1	1
1	1	0	1	1	0	1	1
1	1	1	0	0	0	0	0

Excitation table:

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

For Y,

A, B, X

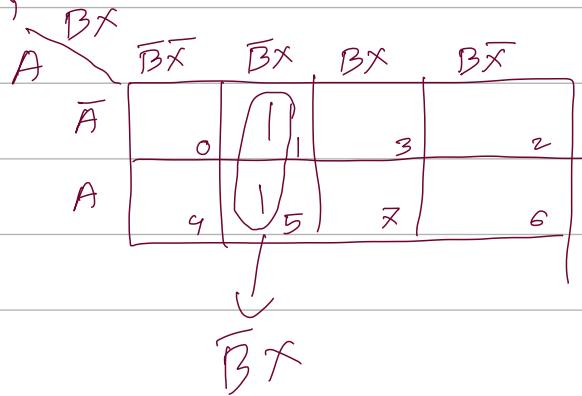

$$Y = \bar{B}X$$

for  $D_A$ ,

$\bar{A}$	$\bar{B}X$	$\bar{B}X$	$BX$	$BX$
0	1	3	2	1
1	0	1	2	0

for  $D_B$ ,

$\bar{A}$	$\bar{B}X$	$\bar{B}X$	$BX$	$BX$
0	0	1	3	2
1	1	0	2	0

$$D_A = A\bar{B} + \bar{B}X$$

$$D_B = \bar{B}X + \bar{A}X + A\bar{B}X$$

