

BRAC UNIVERSITY
Department of Computer Science and Engineering
CSE 260: Digital Logic Design

Examination: Quiz 3
 Duration: 25 Minutes

Semester: Spring 2025
 Full Marks: 15


Name: <u>Solution</u>	ID: _____
-----------------------	-----------

Note: You must mention MSB, LSB in case of all the input and outputs.

1. CO3	Build a 3 input OR gate using three 4:1 MUX(s). (Consider A,B,C as inputs where A is MSB and C is LSB)	[8]
2. CO3	Build Excess-4 to BCD converter using Encoder-Decoder.	[7]

	A	B	C	A+B+C
0	0	0	0	0
1	0	0	1	1
2	0	1	0	1
3	0	1	1	1
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

$$F(A,B,C) = \sum (1,2,3,4,5,6,7)$$


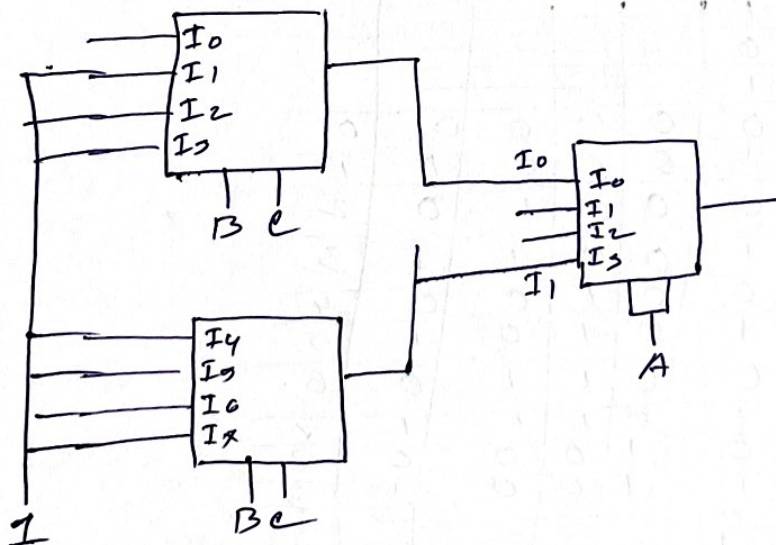


2

BED $\rightarrow 0-9 \rightarrow 9+4=13$

\downarrow
1001
4 bit

\downarrow
1101
4 bit

  

	A	B	C	D	W	X	Y	Z	
0	0	0	0	0					
1	0	0	0	1					
2	0	0	1	0					
3	0	0	1	1					
4	0	1	0	0	0	0	0	0	0
5	0	1	0	1	0	0	0	1	1
6	0	1	1	0	0	0	1	0	2
7	0	1	1	1	0	0	1	1	3
8	1	0	0	0	0	1	0	0	4
9	1	0	0	1	0	1	0	1	5
10	1	0	1	0	0	1	1	0	6
11	1	0	1	1	0	1	1	1	7
12	1	1	0	0	1	0	0	0	8
13	1	1	0	1	1	0	0	1	9
14	1	1	1	0					
15	1	1	1	1					