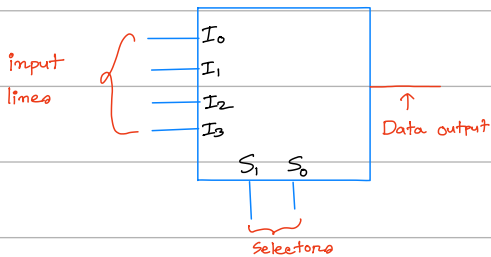


Multiplexer



$4:1$ mux - 2 selectors
 \uparrow
 $2^n:1$ mux - n selectors
 \uparrow
 number of input lines

Large Mux:

Build $8:1$ mux using two $4:1$ and one $2:1$ mux.


$8:1 = 2^3:1$

So, 3 selector bits = $S_2 S_1 S_0$


\downarrow MSB \downarrow LSB
 S_2 S_1 S_0

Muxes that are in the same level their selector(s) will be shared.

Start assigning the selector bits from the right side. (MSB)

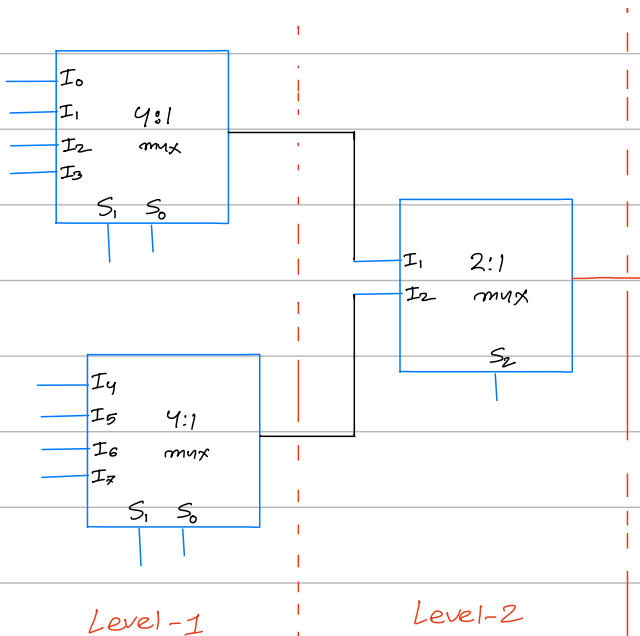

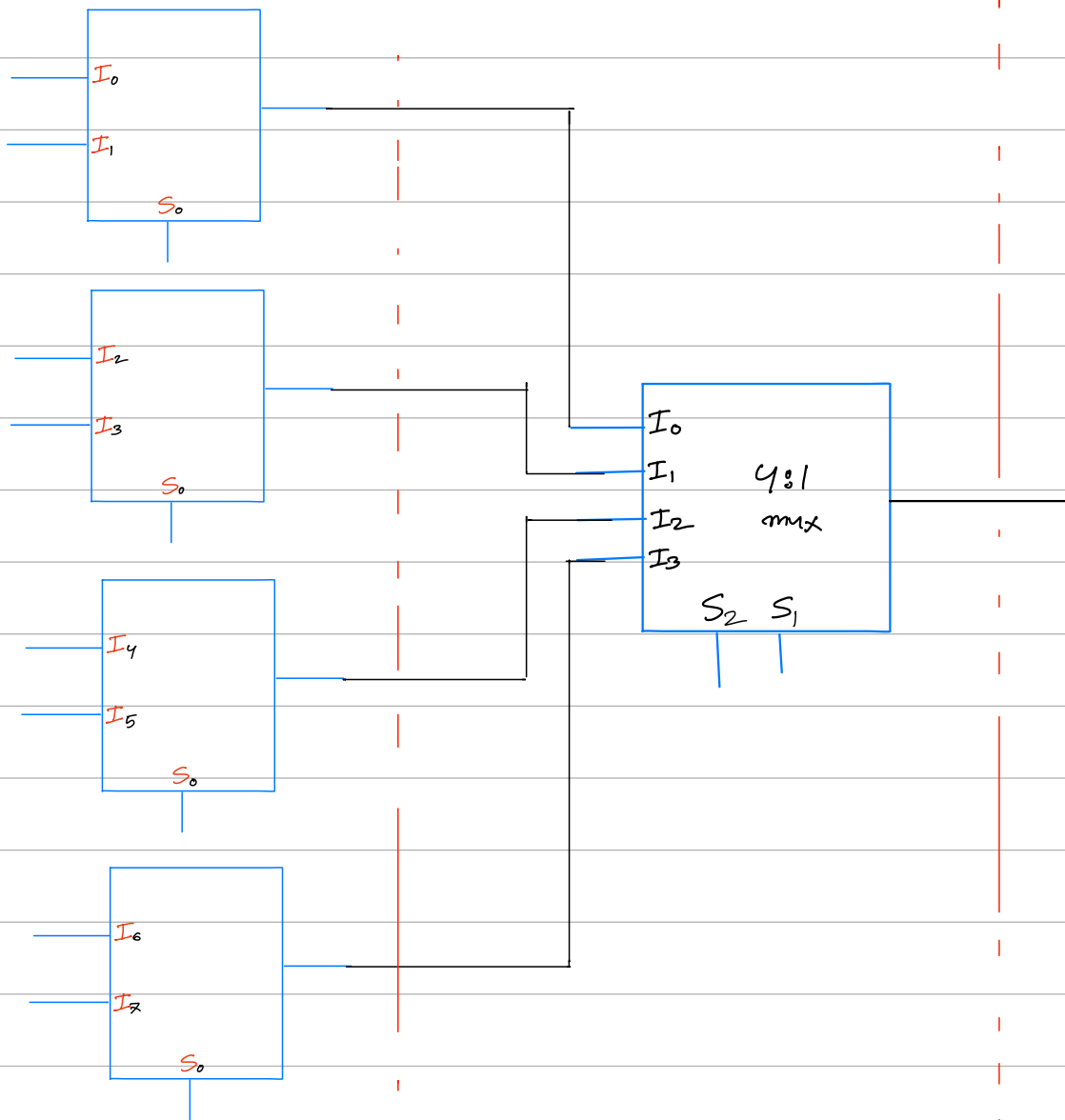Build 8:1 mux using four 2:1 and one 4:1 mux.




Level-1

Level-2


Implement a 2:1 mux using 4:1 mux.

$\Rightarrow 2:1 = 2^1:1$; 1 selector

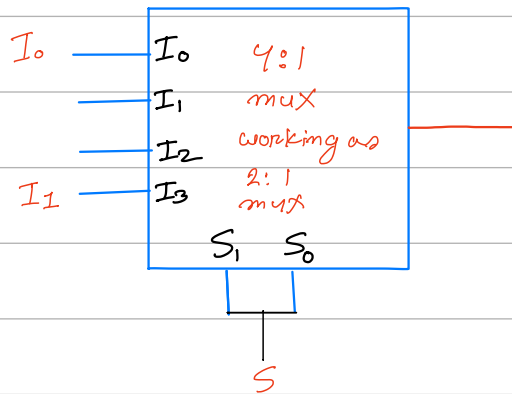


Function implementation using Mux

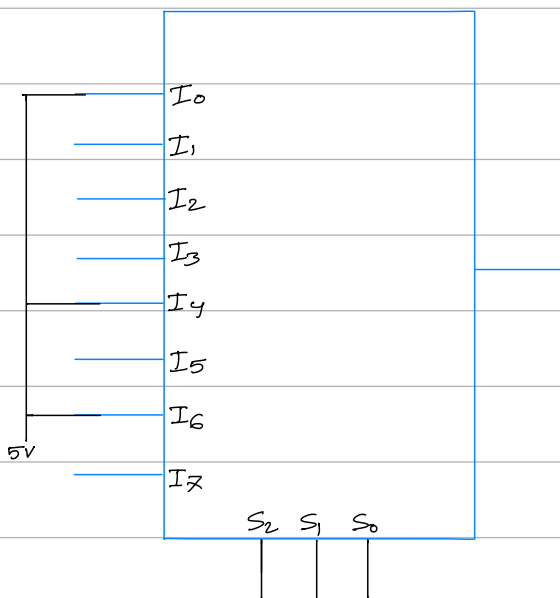$F = \Sigma(0, 4, 6)$; implement the given function using 8:1 mux.



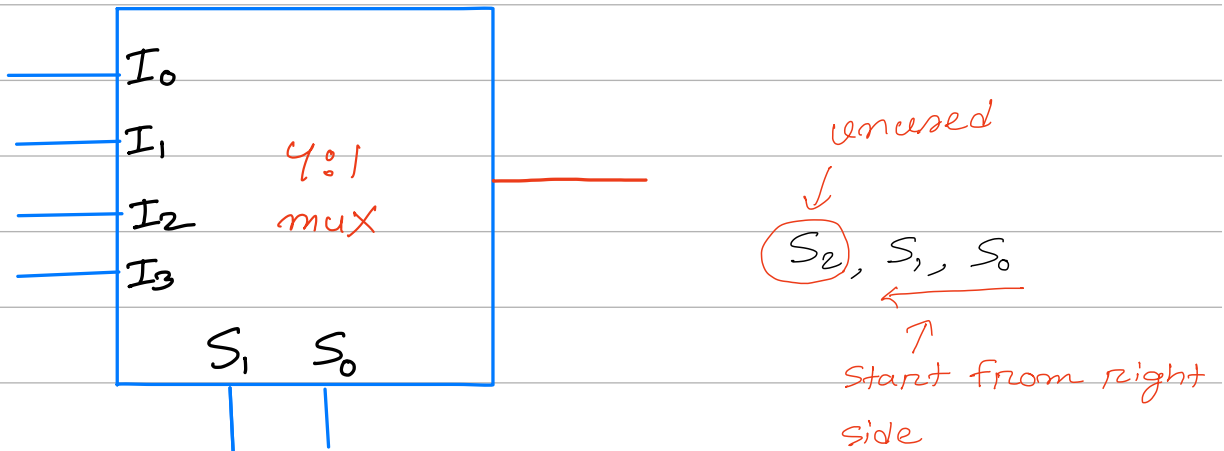$F(S_2, S_1, S_0) = \Sigma(0, 4, 6)$; implement the given function using a 4:1 mux.



Build a table:

column wise: All the input values of the Mux you are currently using.

	I_0	I_1	I_2	I_3
A'	0	1	2	3
A	4	5	6	7

Row-wise: $A + A' = 1$

0 A 0


All the combinations possible for the unused variable(s)

Circle rules:

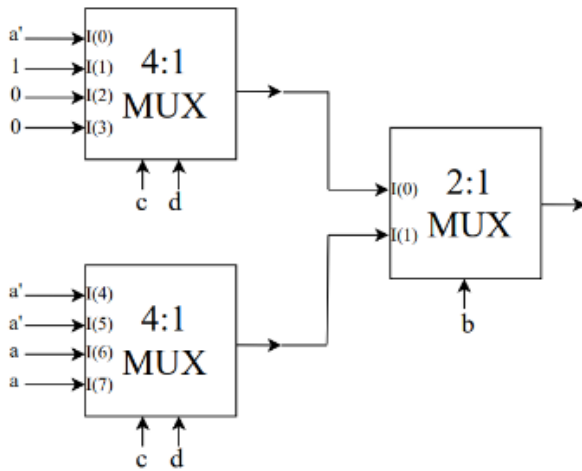- (i) If in a column there is no circle
Output = 0
- (ii) If in a column all the cells ^{are} circled
Output = 1
- (iii) If some of the cells are circled then take the row variable combination of each cell and "+" them. [Simplify if possible]
- (iv) In case of a single cell circled, just take the row variable combination of that cell.

$$F(a,b,c,d)=\sum(0,1,4,5,9,14,15)$$

Implement the above boolean function using two 4:1 MUX(s) and one 2:1 MUX.



	I(0)	I(1)	I(2)	I(3)	I(4)	I(5)	I(6)	I(7)
a'	0	1	2	3	4	5	6	7
a	8	9	10	11	12	13	14	15
	a'	1	0	0	a'	a'	a	a